

Processor Design

Simple RISC
ISA

Basic Computer Architecture

Outline

- * Overview of a Processor
- * Detailed Design of each Stage
- * The Control Unit
- * Microprogrammed Processor
- * Microassembly Language
- * The Microcontrol Unit



Processor Design

- * The aim of **processor design**


32 bits

- * **Implement** the entire SimpleRisc ISA
- * **Process** the binary format of instructions
- * Provide as much of **performance** as possible

- * **Basic Approach**


- * Divide the processing into stages
- * Design each stage separately

A Car Assembly Line

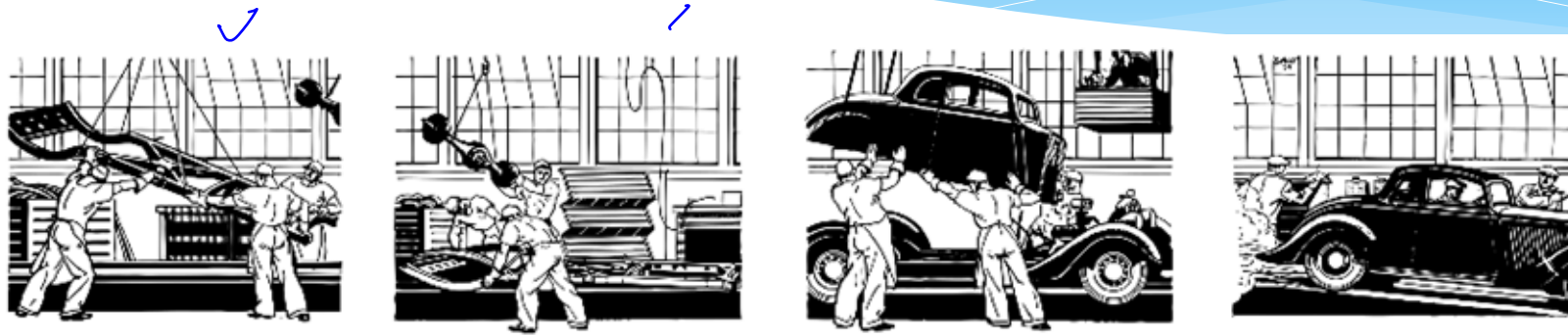

- * Similar to a car **assembly line**
 - * Cast raw **metal** into the **chassis** of a car
 - * Build the **Engine**
 - * Assemble the **engine** and the **chassis**
 - * Place the **dashboard**, and **upholstery**

A Processor Divided Into Stages

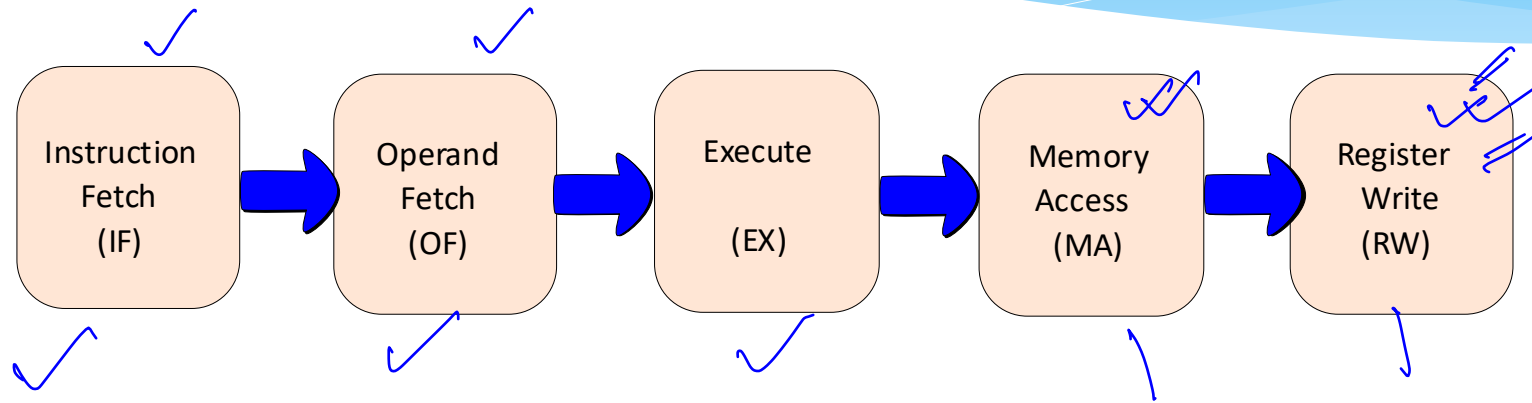

* Instruction **Fetch** (IF)

- * **Fetch** an instruction from the instruction memory
- * **Compute** the address of the next instruction

Operand Fetch (OF) Stage

* Operand Fetch (OF)


* **Decode** the instruction (break it into fields)

* **Fetch** the register operands from the register file


* Compute the **branch target** (PC + offset)

* Compute the **immediate** (16 bits + 2 bit modifiers)

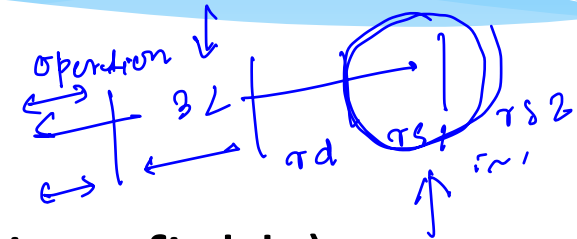
* ~~Generate **control signals** (we will see later)~~



word \Rightarrow 4 bytes

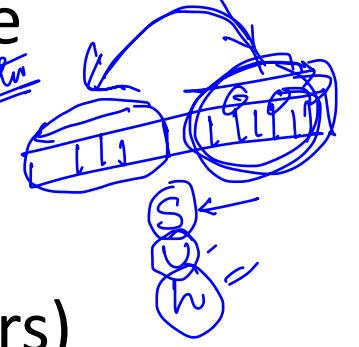


18 bits

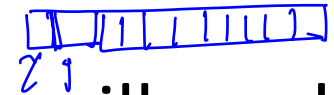

Recap from SimpleRISC ISA

Immediate Format

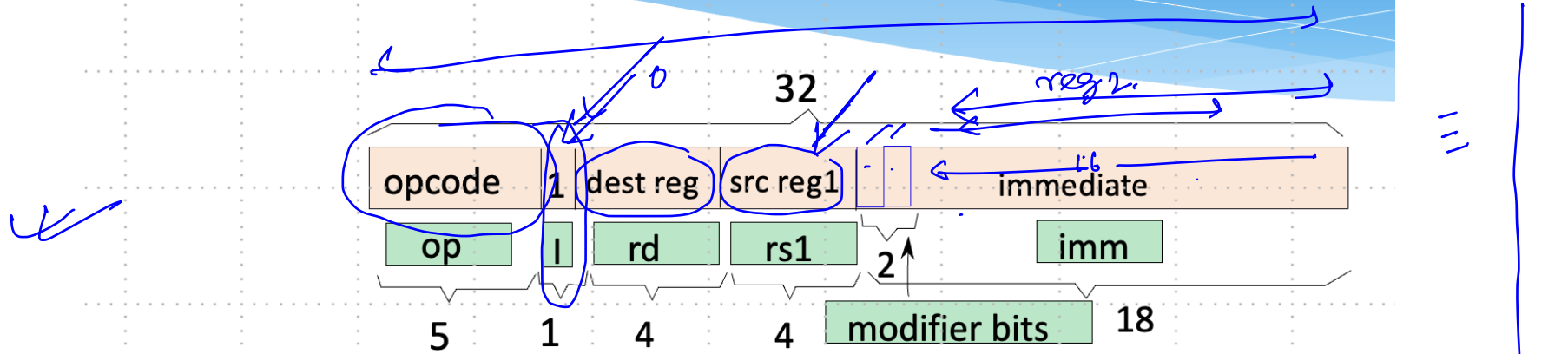

- * opcode → type of the instruction
- * **I** bit → 1 (second operand is an immediate)
- * dest reg → rd
- * **source register 1** → rs1
- * **Immediate** → imm
- * **modifier bits** → 00 (default), 01 (u), 10 (h)

Execute (EX) Stage

* The EX Stage

- * Contains an **Arithmetic-Logical Unit (ALU)** ✓

- * This unit can perform all arithmetic operations (add, sub, mul, div, cmp, mod), and **logical** operations (and, or, not)

b →
beq →
bgt →

- ✓ * Contains the **branch** unit for computing the branch condition (beq, bgt)

A - B

- * Contains the **flags** register (updated by the cmp instruction)

cmp A-B


Special **flags** register → contains the result of the last comparison

* flags.E = 1 (equality), flags.GT = 1 (greater than)

MA and RW Stages


- * MA (Memory Access) Stage

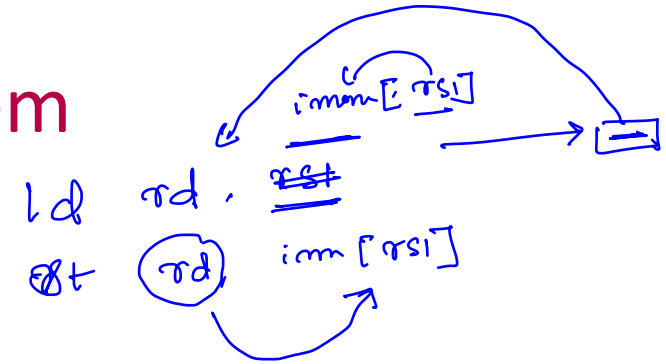- * Interfaces with the memory system
- * Executes a load or a store




- * RW (Register Write) Stage

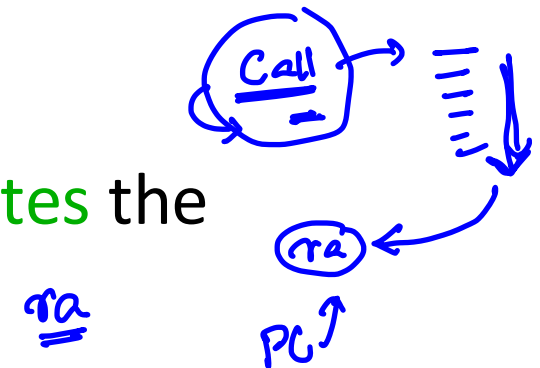- * Writes to the register file
- * In the case of a call instruction, it writes the return address to register, ra




Outline

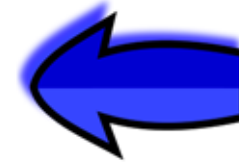
- * Outline of a Processor
- * Detailed Design of each Stage
- * The Control Unit
- * Microprogrammed Processor
- * Microassembly Language
- * The Microcontrol Unit



Instⁿ Fetch Stage

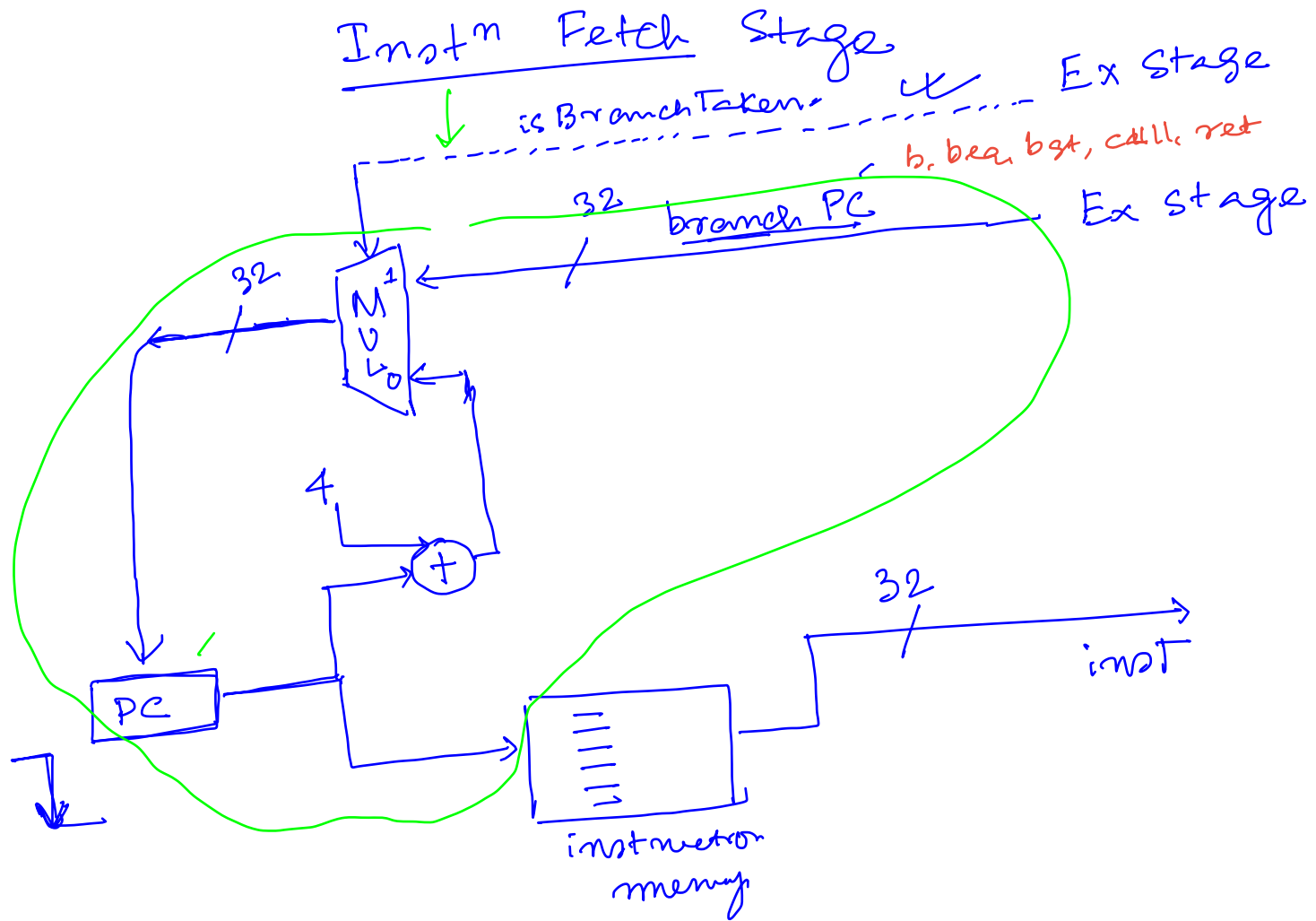

Instruction Fetch (IF) Stage

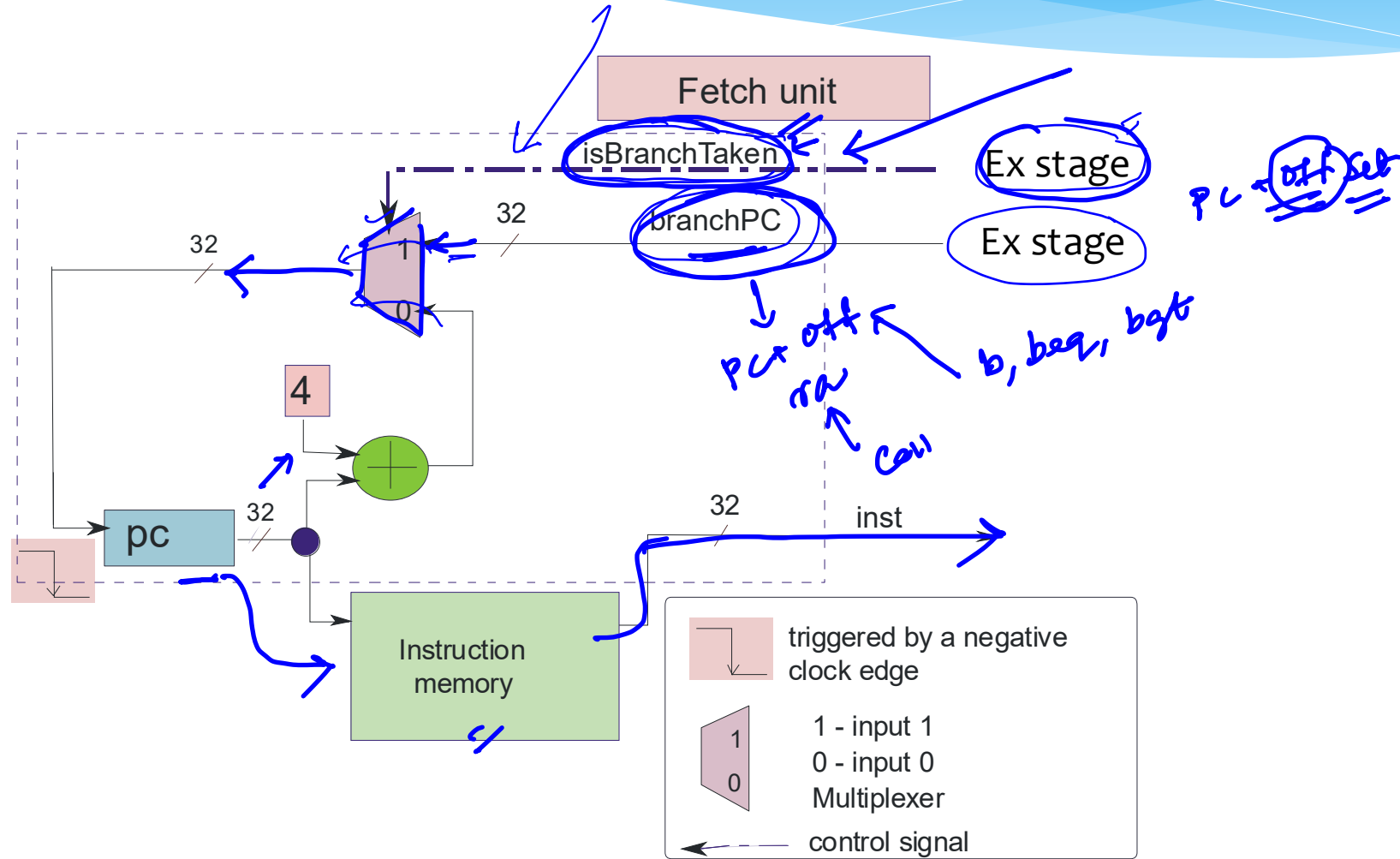

The Fetch unit

- * The **pc** register contains the **program counter** (negative edge triggered)
- * We use the **pc** to access the instruction memory
- * The **multiplexer** chooses between
 - * $pc + 4$
 - * $branchTarget$ ✓
- * It uses a control signal \rightarrow **isBranchTaken** ^{1/0}

isBranchTaken

- * isBranchTaken is a **control** signal
 - * It is generated by the EX unit
- * Conditions on isBranchTaken = 1


Instruction	Value of <i>isBranchTaken</i>
non-branch instruction	0
✓ <i>call</i>	1
✓ <i>ret</i>	1
✓ <i>b</i>	1
✓ <i>beq</i>	branch taken – 1 branch not taken – 0
✓ <i>bgt</i>	branch taken – 1 branch not taken – 0

$\frac{\text{flags.E} = 1}{\text{flags.gt} = 1}$

Data Path and Control Path


- * The **data path** consists of all the elements in a processor that are dedicated to storing, retrieving, and processing data such as **register files, memory, and the ALU**.
- * The **control path** primarily contains the **control unit**, whose role is to generate the appropriate signals to control the **movement of instructions**, and **data** in the data path.

Control Path


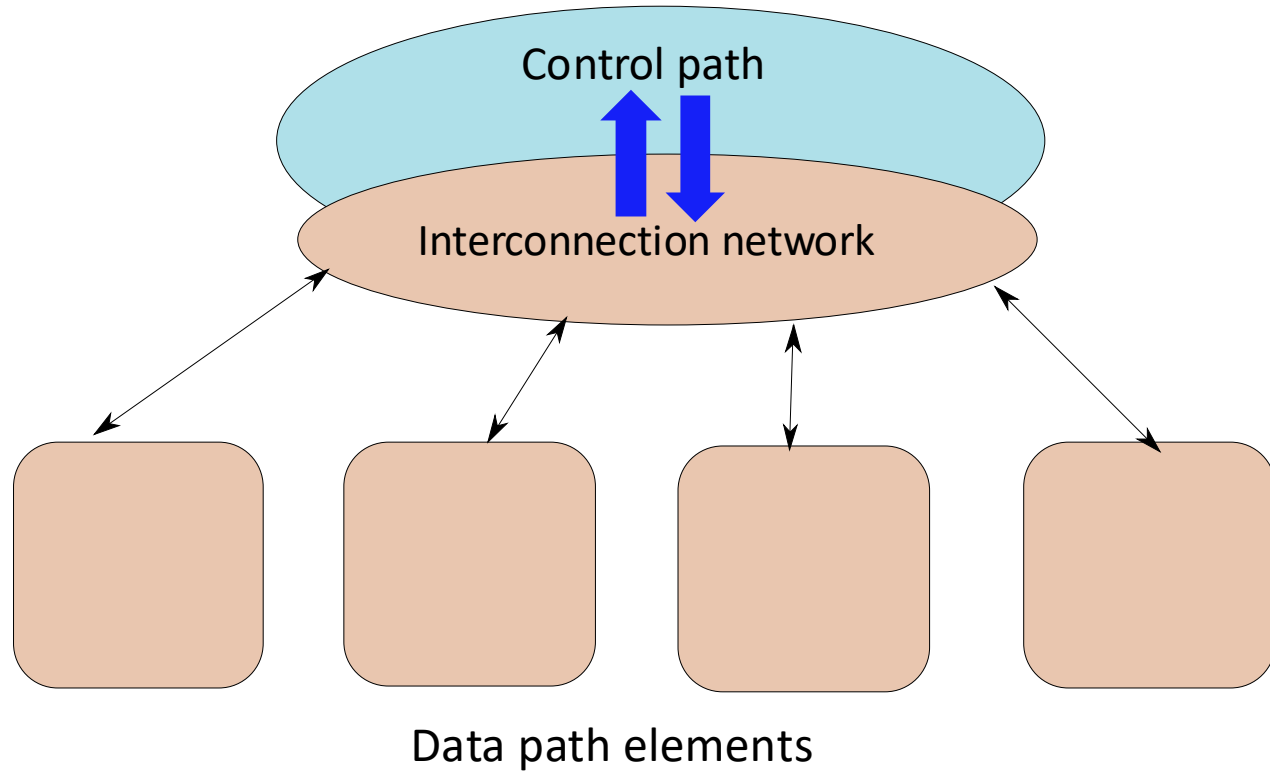


We will currently look at the hardwired control path.


Operand Fetch Unit

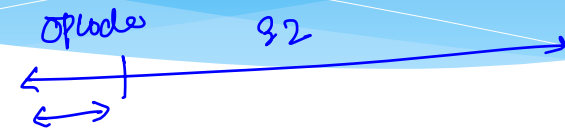

Inst.	Code	Format	Inst.	Code	Format
add	00000	add rd, rs1, (rs2/imm)	lsl	01010	lsl rd, rs1, (rs2/imm)
sub	00001	sub rd, rs1, (rs2/imm)	lsr	01011	lsr rd, rs1, (rs2/imm)
mul	00010	mul rd, rs1, (rs2/imm)	asr	01100	asr rd, rs1, (rs2/imm)
div	00011	div rd, rs1, (rs2/imm)	nop	01101	nop
mod	00100	mod rd, rs1, (rs2/imm)	ld	01110	ld rd, imm[rs1]
cmp	00101	cmp rs1, (rs2/imm)	st	01111	st rd, imm[rs1]
and	00110	and rd, rs1, (rs2/imm)	beq	10000	beq offset
or	00111	or rd, rs1, (rs2/imm)	bgt	10001	bgt offset
not	01000	not rd, (rs2/imm)	b	10010	b offset
mov	01001	mov rd, (rs2/imm)	call	10011	call offset
			ret	10100	ret

 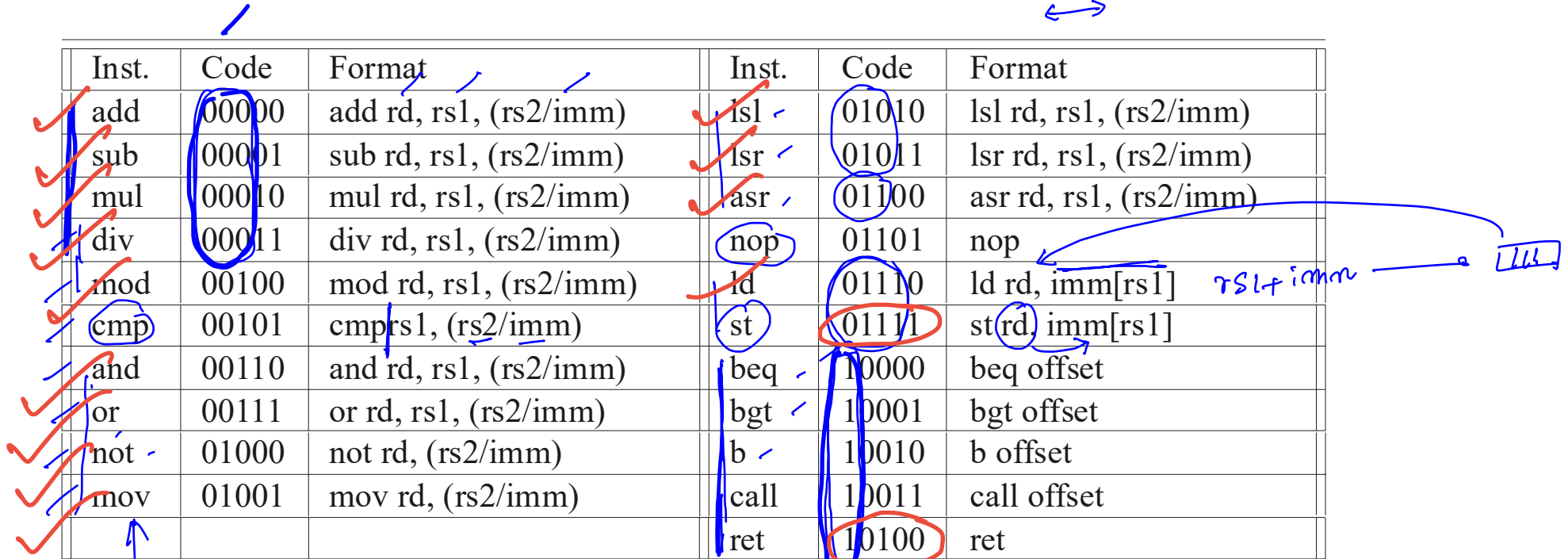


is Wb

 


Instruction Formats

Format	Definition				
branch	op (28-32)	offset (1-27)	Word offset		
register	op (28-32)	I (27)	rd (23-26)	rs1 (19-22)	rs2 (15-18)
immediate	op (28-32)	I (27)	rd (23-26)	rs1 (19-22)	imm (1-18)
<i>op</i> → opcode, <i>offset</i> → branch offset, <i>I</i> → immediate bit, <i>rd</i> → destination register <i>rs1</i> → source register 1, <i>rs2</i> → source register 2, <i>imm</i> → immediate operand					

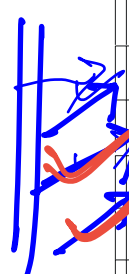


U.S. ← 16

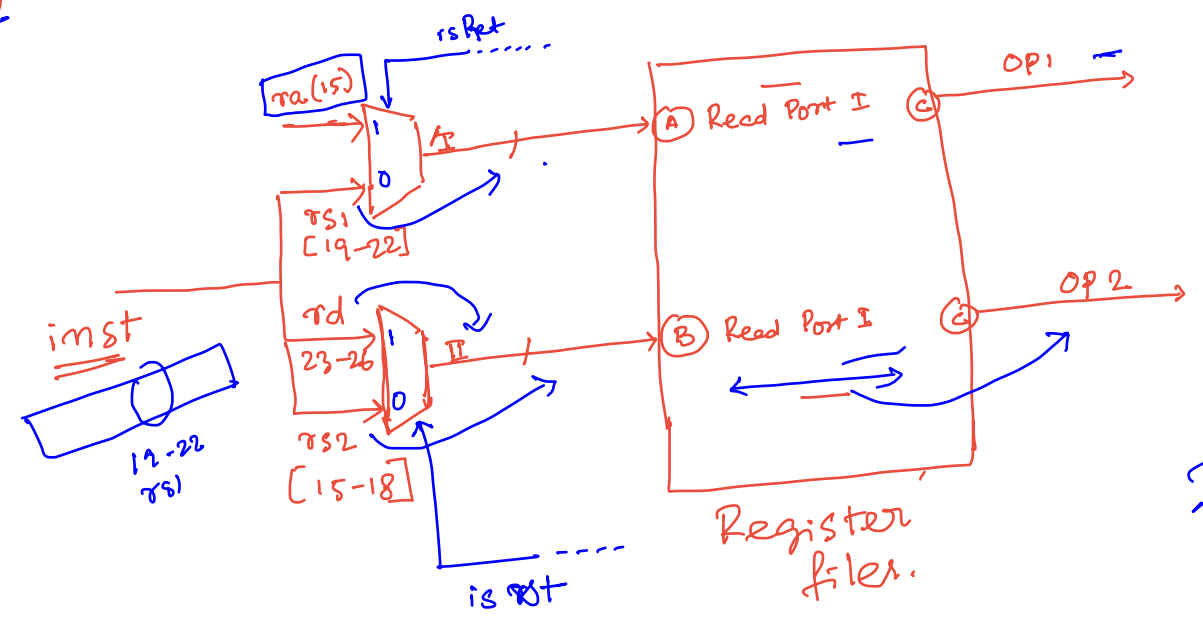Register File read
 Immediate
 branch Target



st = rd, imm[rs1]

Register File Read

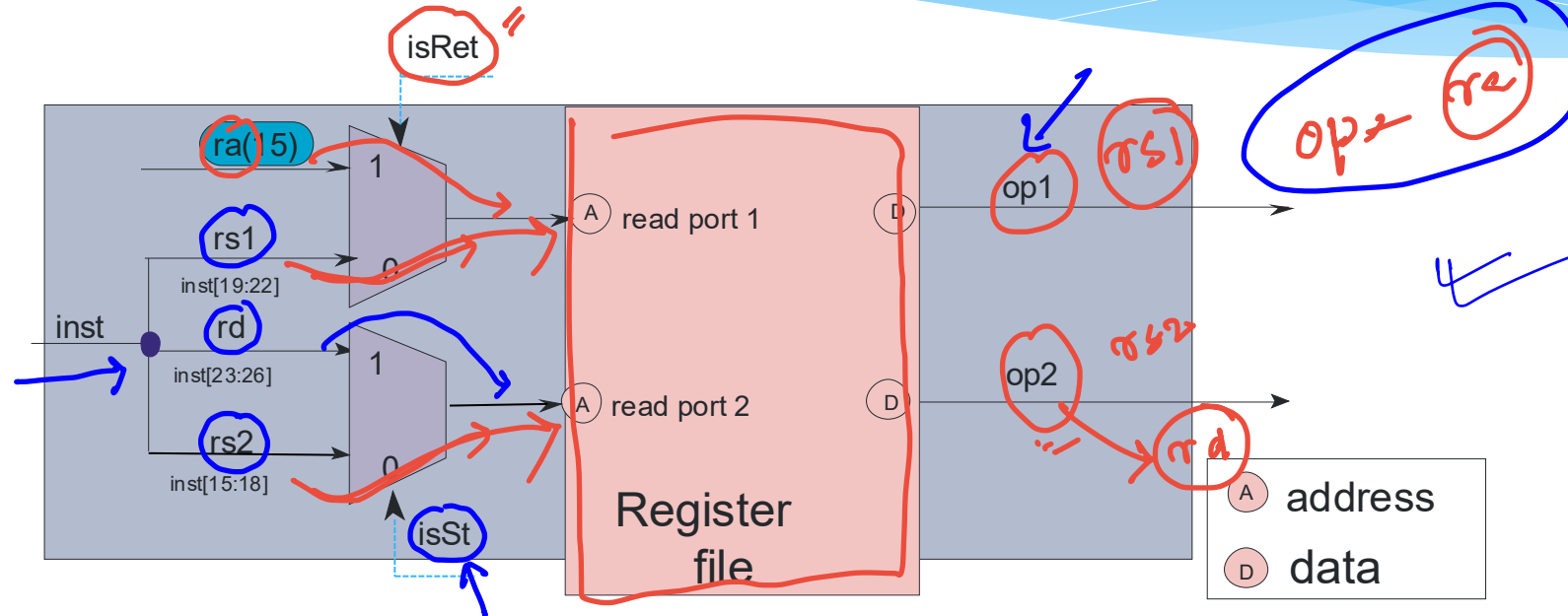


- * **First input** → *rs1* or *ra(15)* (ret instruction)
- * **Second input** → *rs2* or *rd* (store instruction)

Register File Access


- * The **register file** has two **read ports**
 - * 1st Input
 - * 2nd Input
- * The two outputs are **op1**, and **op2**
 - * **op1** is the **branch target (return address)** in the case of a **ret** instruction, or **rs1**
 - * **op2** is the value that needs to be stored in the case of a **store** instruction, or **rs2**

Immediate and Branch Unit

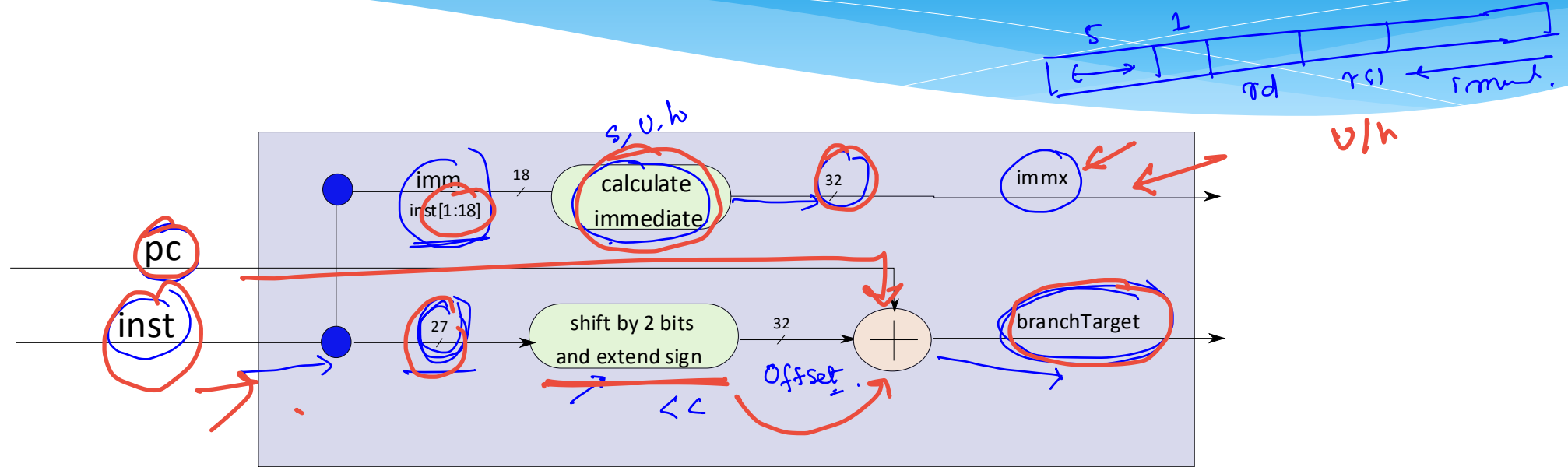


- * Compute **immx** (extended immediate), **branchTarget**, irrespective of the **instruction format**.
- * For the **branchTarget** we need to choose between the embedded target and op1 (ret)

OF Unit

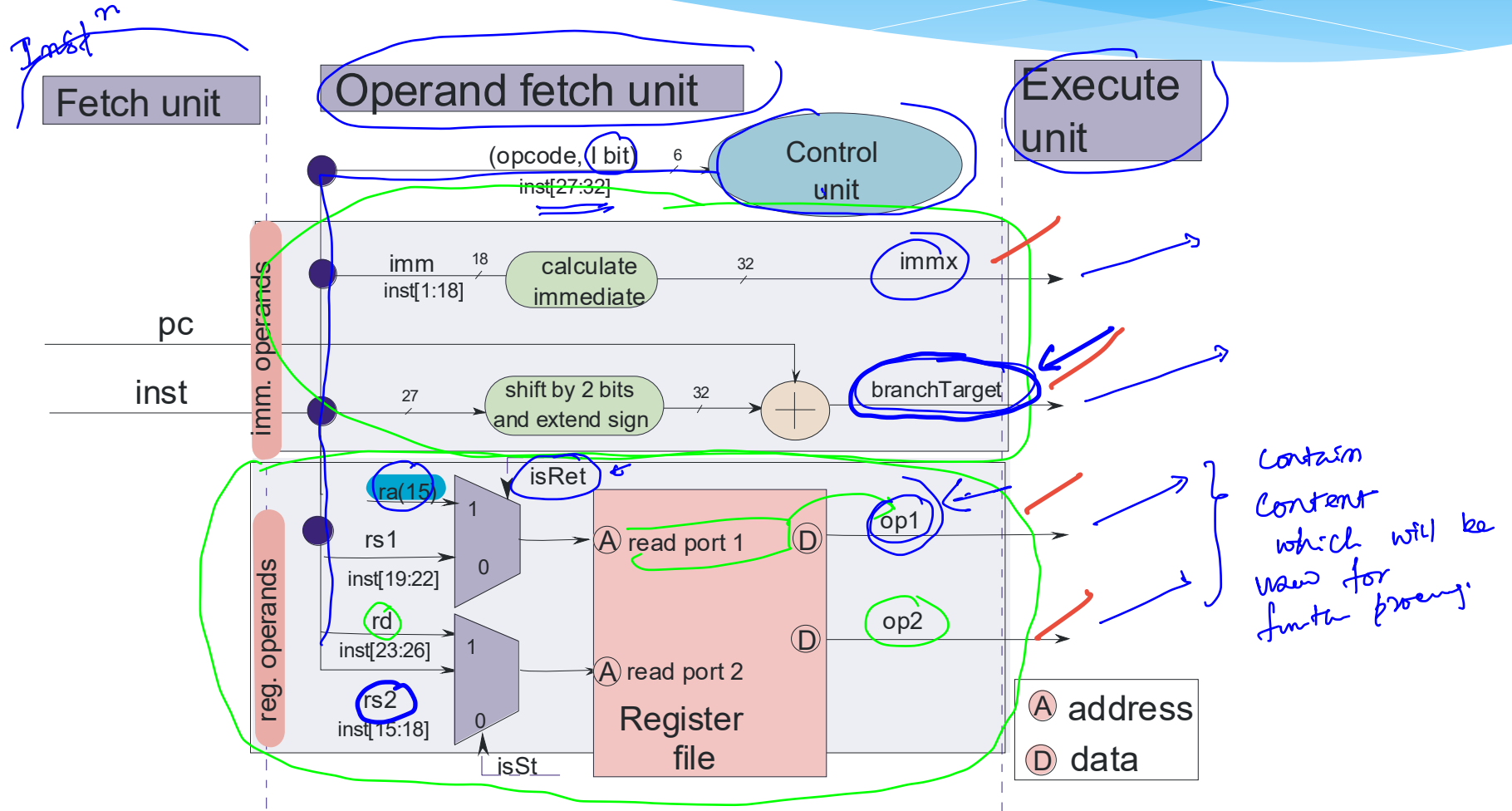


EX Stage – Branch Unit

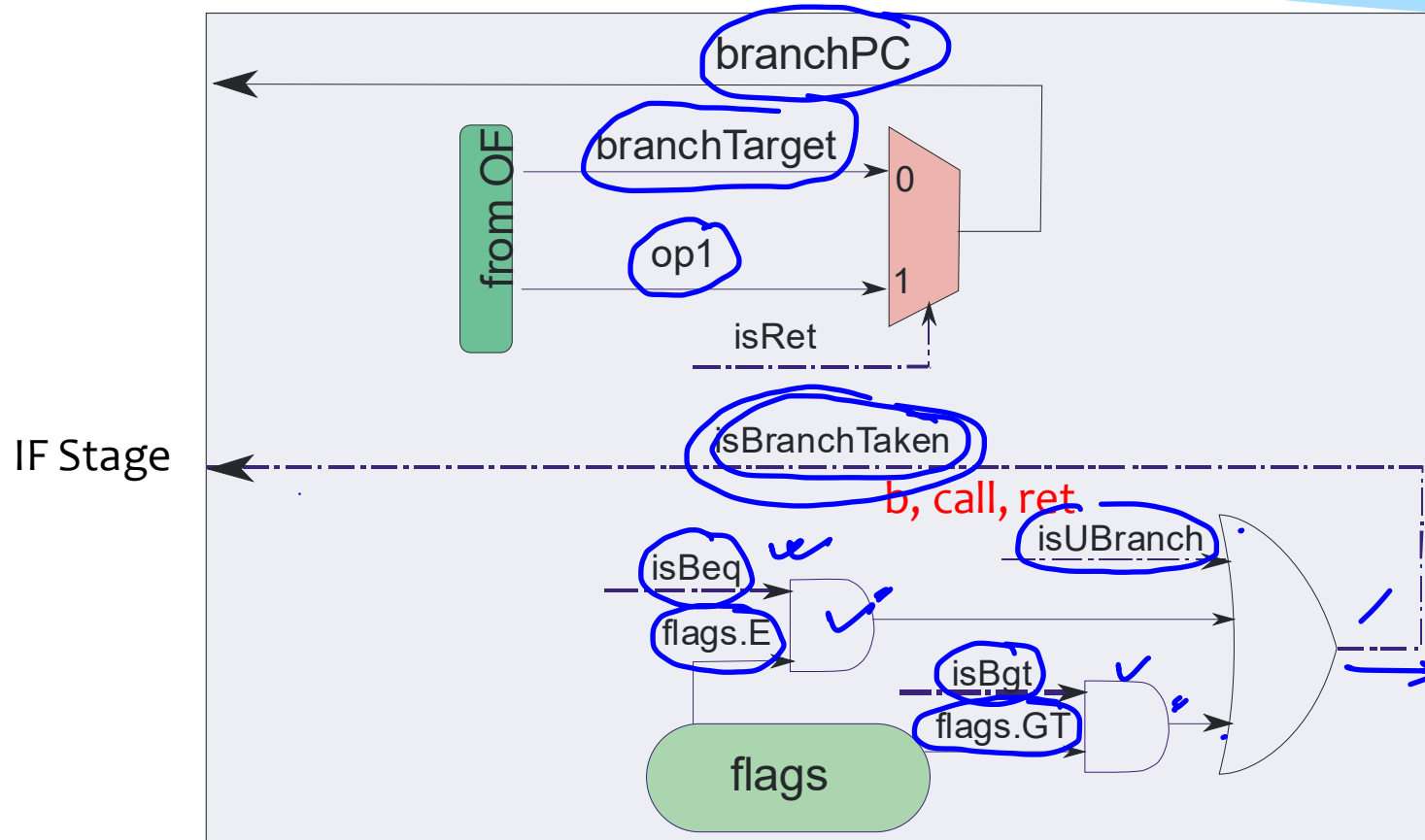

Generates the isBranchTaken Signal

ALU


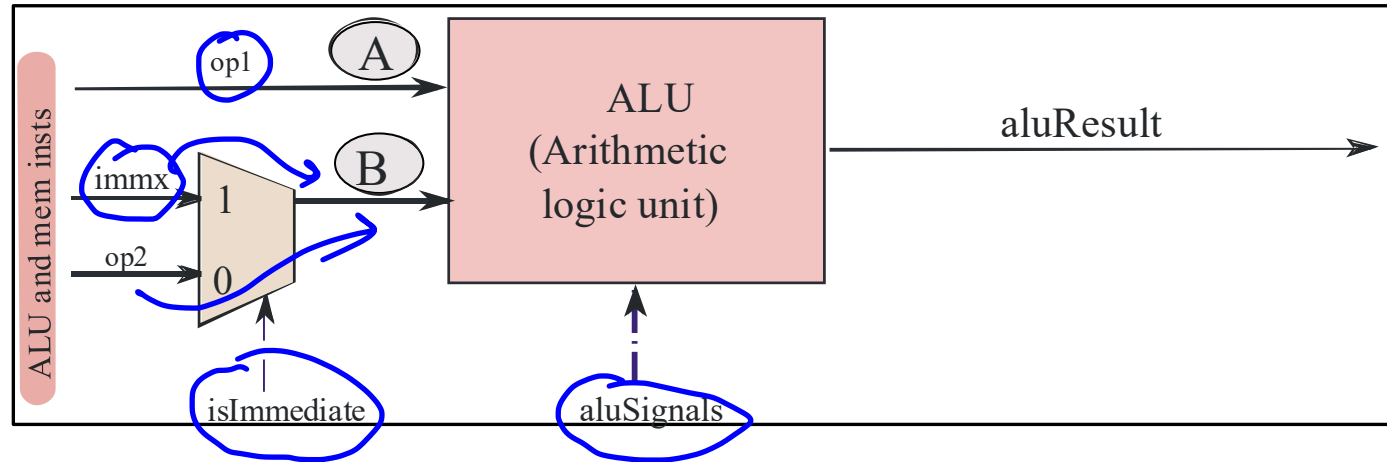


Choose between immx and op2 based on the value of the I bit

Disabling some Inputs


- * We do not want all the **units** of the ALU to be **active** at the same time because of we want to save **power**
- * The **instruction** will only use 1 **unit**
- * **Power** is dissipated when the **inputs** or **outputs** make a **transition** ($0 \rightarrow 1, 1 \rightarrow 0$)
 - * We shall avoid a **transition** by not letting the new **inputs** to propagate to **units** that do not require them
 - * They will thus have the **old inputs** (**no** switching)

Use a Transmission Gate

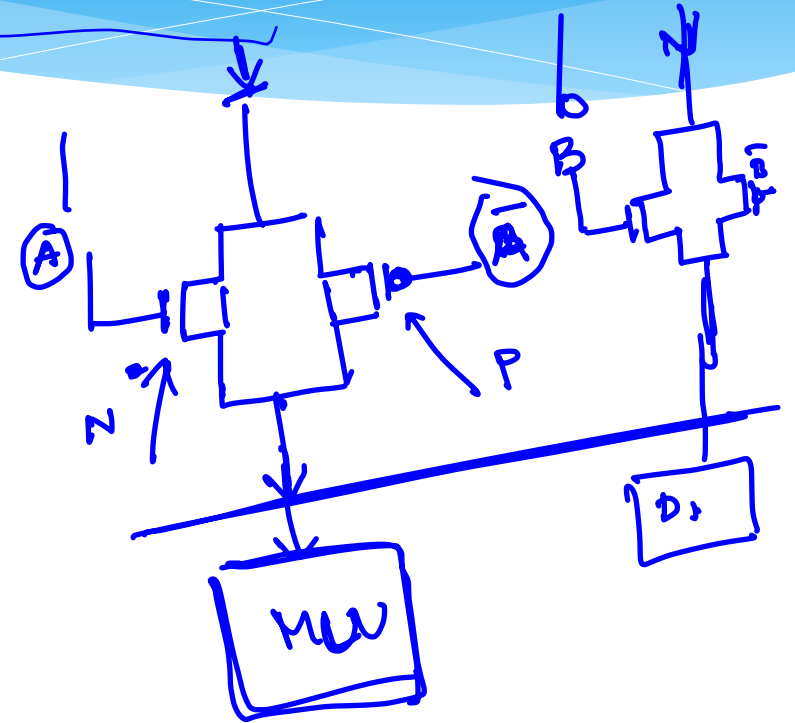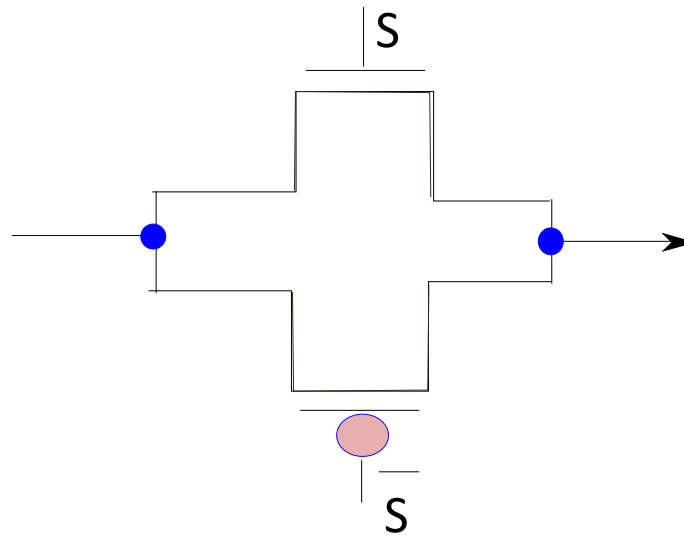


- * output = input (if $S = 1$)
- * Otherwise, the **output** is totally disconnected from the **input**


EX Unit

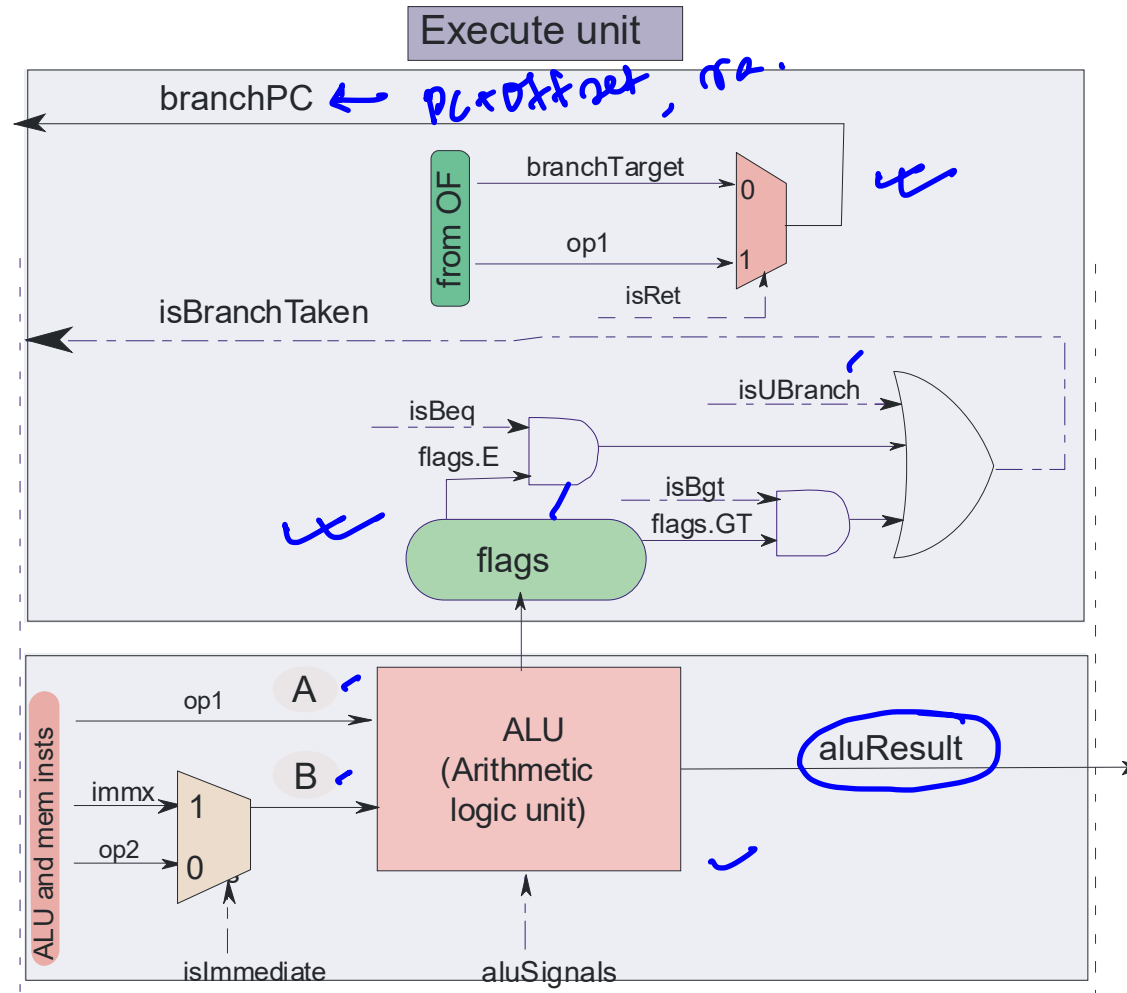


MA Unit

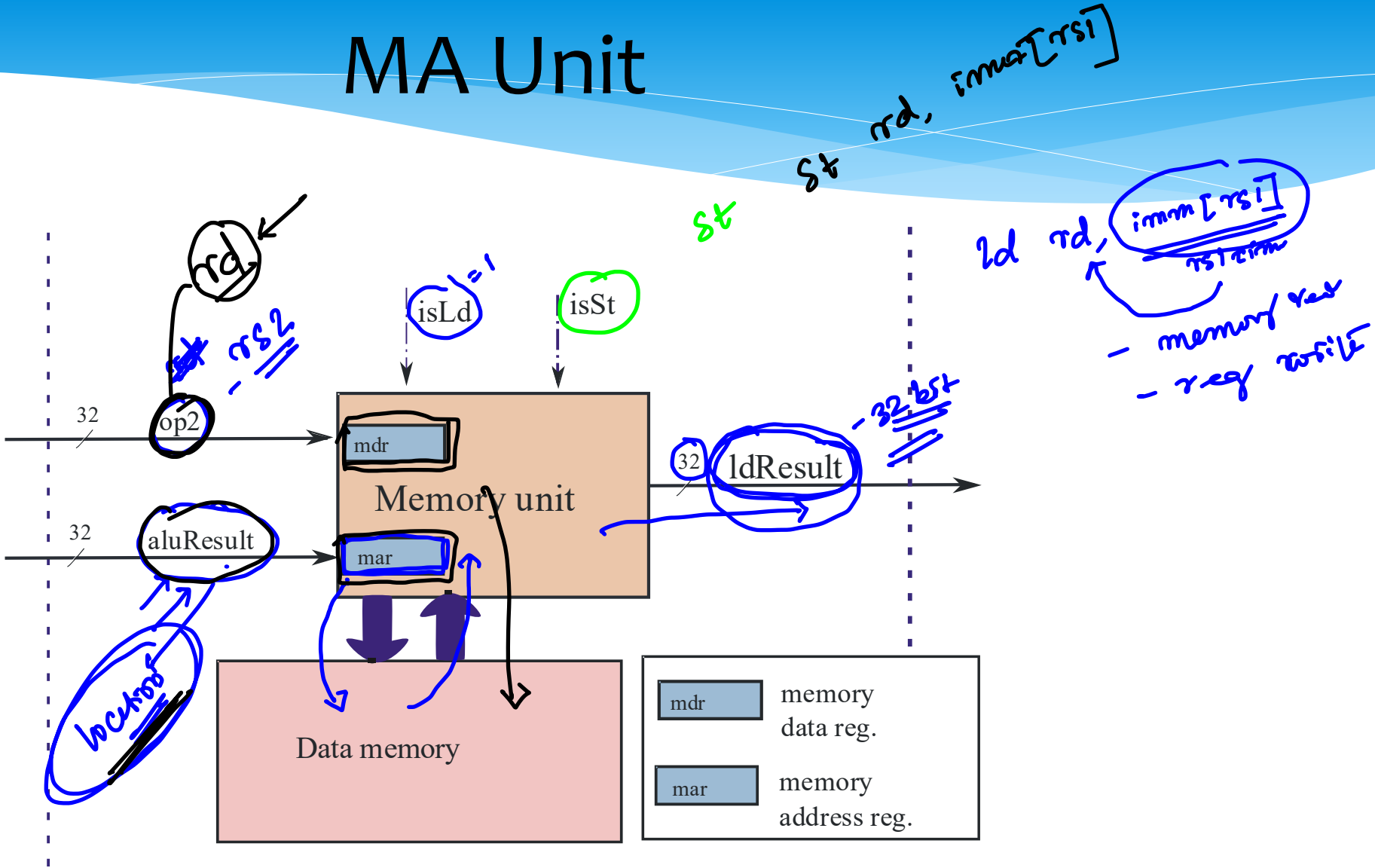

RW Unit

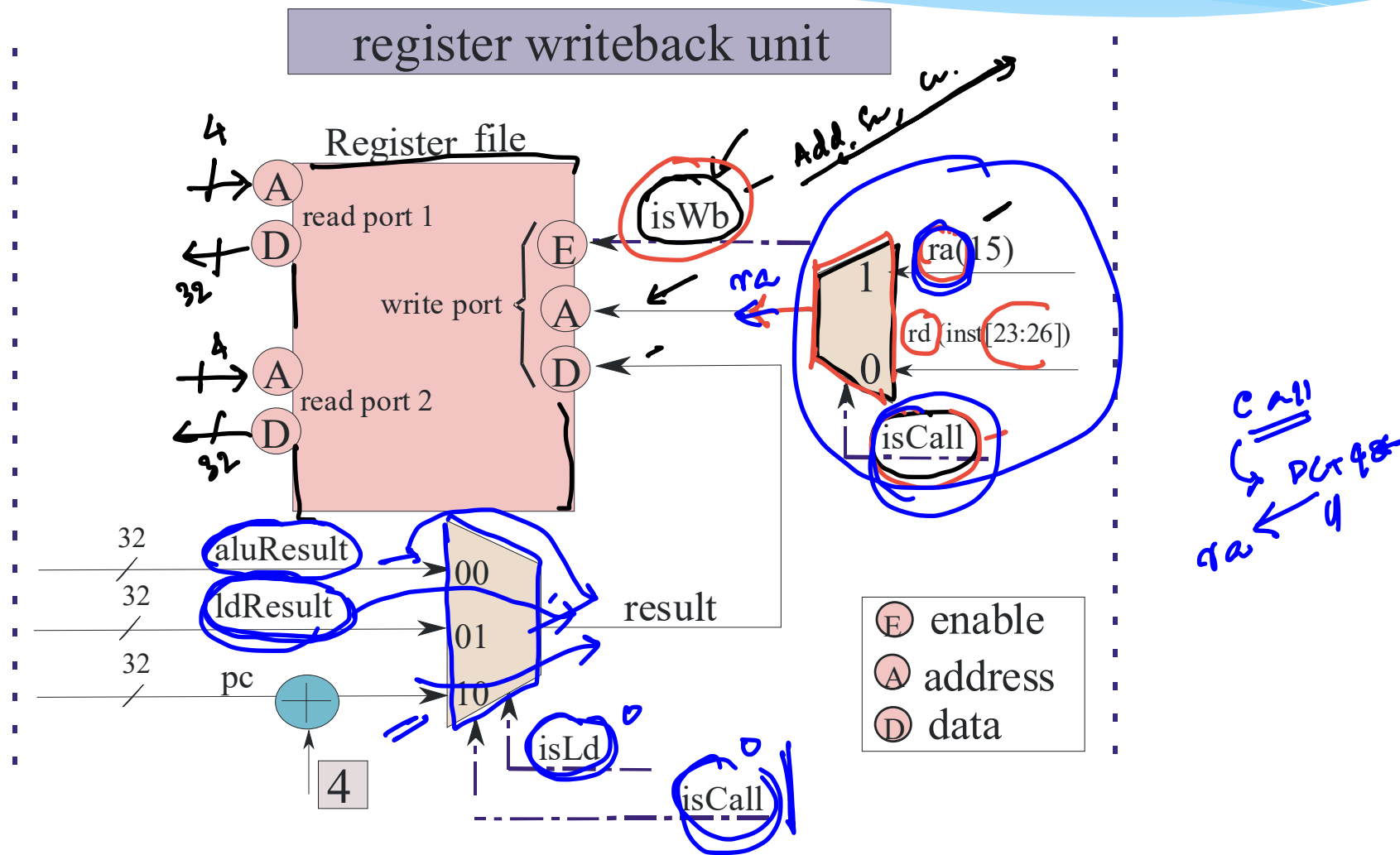

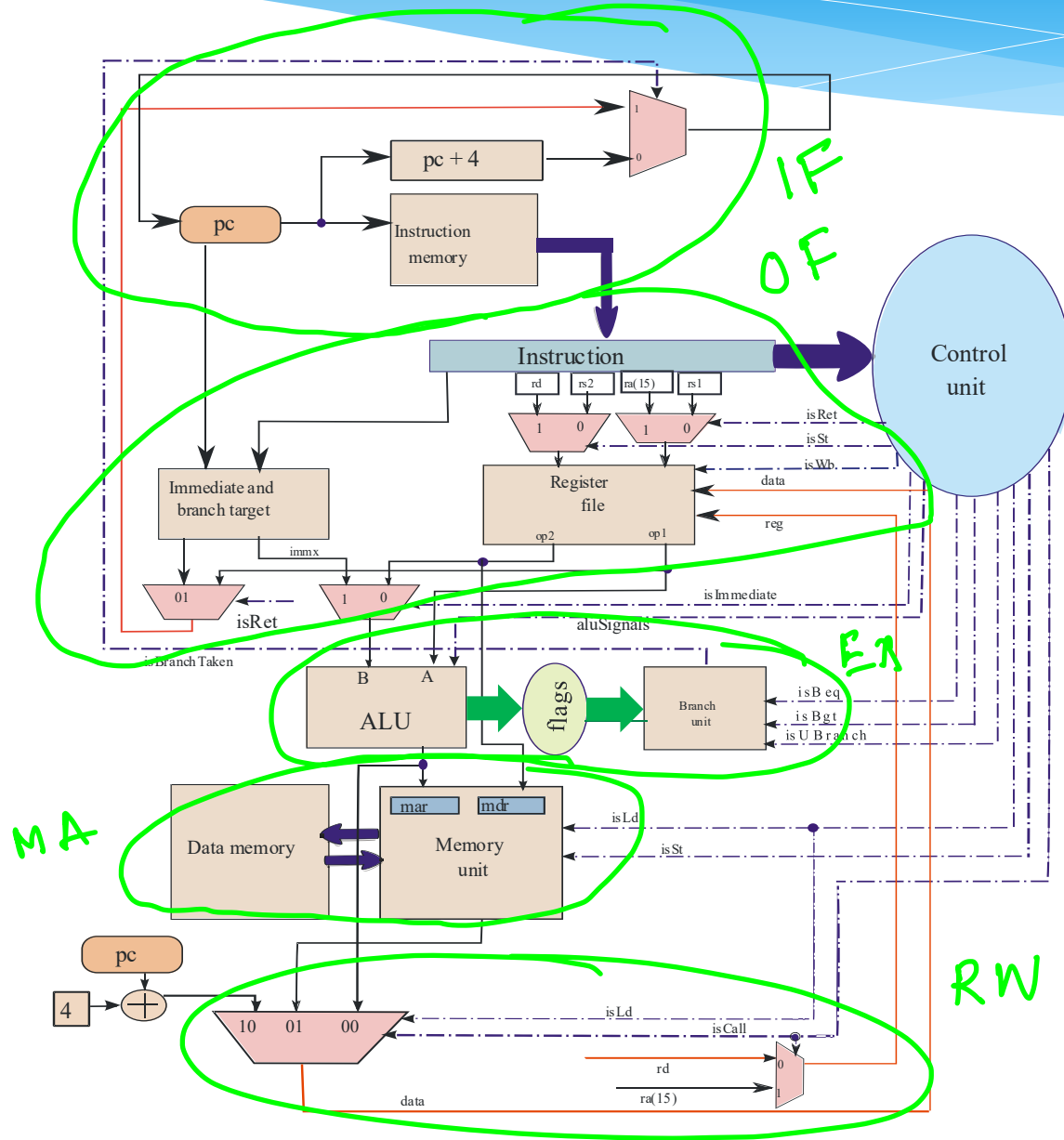


Outline

- * Outline of a Processor
- * Detailed Design of each Stage
- * The Control Unit
- * Microprogrammed Processor
- * Microassembly Language
- * The Microcontrol Unit



The Hardwired Control Unit

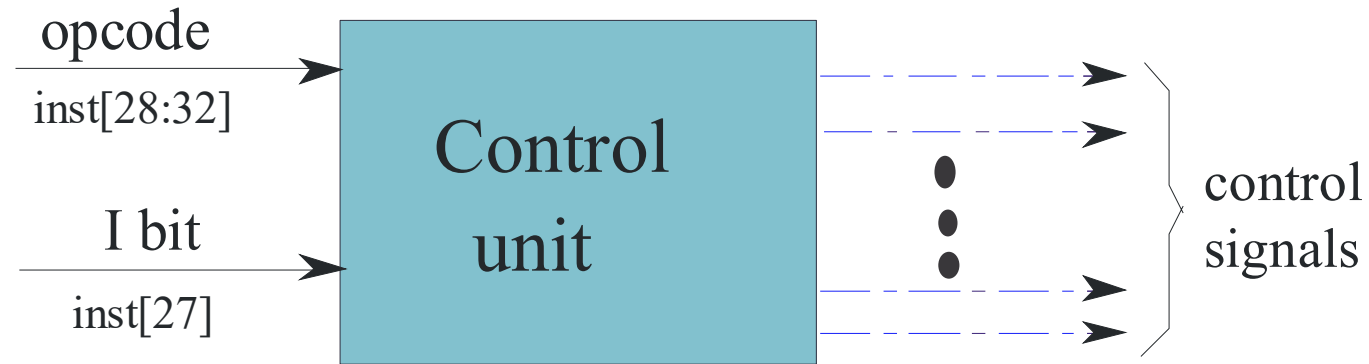

- * Given the **opcode** and the **immediate** bit
 - * It generates all the **control signals**


Control Signals

SerialNo.	Signal	Condition
1	<i>isSt</i> ✓	Instruction: <i>st</i>
2	<i>isLd</i> ✓	Instruction: <i>ld</i>
3	<i>isBeq</i> ✓	Instruction: <i>beq</i>
4	<i>isBgt</i> ✓	Instruction: <i>bgt</i>
5	<i>isRet</i> ✓	Instruction: <i>ret</i>
6	<i>isImmediate</i> ✓	<i>I</i> bit set to 1
7	<i>isWb</i> ✓	Instructions: <i>add, sub, mul, div, mod, and, or, not, mov, ld, lsl, lsr, asr, call</i>
8	✓ <i>isUBranch</i>	Instructions: <i>b, call, ret</i>
9	✓ <i>isCall</i>	Instructions: <i>call</i>


Control Signals – II

		<i>aluSignal</i>
10	<i>isAdd</i> ✓	Instructions: <i>add, ld, st</i>
11	<i>isSub</i> ✓	Instruction: <i>sub</i>
12	<i>isCmp</i> ✓	Instruction: <i>cmp</i>
13	<i>isMul</i>	Instruction: <i>mul</i>
14	<i>isDiv</i>	Instruction: <i>div</i>
15	<i>isMod</i>	Instruction: <i>mod</i>
16	<i>isLsl</i>	Instruction: <i>lsl</i>
17	<i>isLsr</i>	Instruction: <i>lsr</i>
18	<i>isAsr</i>	Instruction: <i>asr</i>
19	<i>isOr</i>	Instruction: <i>or</i>
20	<i>isAnd</i>	Instruction: <i>and</i>
21	<i>isNot</i>	Instruction: <i>not</i>
22	<i>isMov</i>	Instruction: <i>mov</i>

isSt

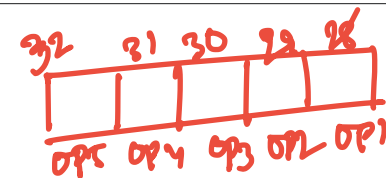

Control signal Logic

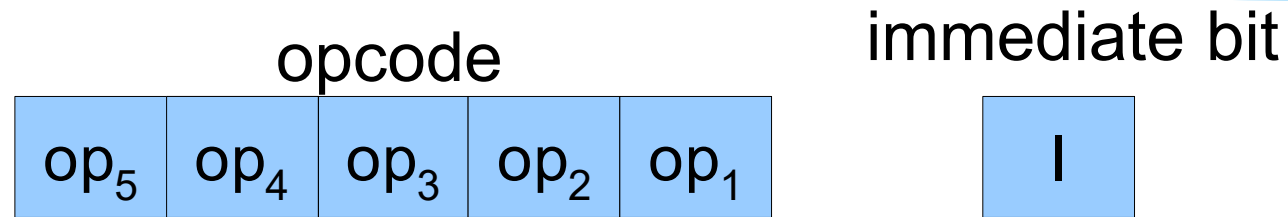

Serial No.	Signal	Condition
1	<i>isSt</i>	$\overline{op_5} \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot \overline{op_1}$
2	<i>isLd</i>	$\overline{op_5} \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot \overline{op_1}$
3	<i>isBeq</i>	$op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot \overline{op_1}$
4	<i>isBgt</i>	$op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot op_1$
5	<i>isRet</i>	$op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot \overline{op_1}$
6	<i>isImmediate</i>	<i>I</i>
7	<i>isWb</i>	$\overline{op_5} + \overline{op_5} \cdot \overline{op_3} \cdot \overline{op_1} \cdot (op_4 + \overline{op_2}) + op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot op_1$
8	<i>isUbranch</i>	$op_5 \cdot \overline{op_4} \cdot (\overline{op_3} \cdot \overline{op_2} + op_3 \cdot \overline{op_2} \cdot \overline{op_1})$
9	<i>isCall</i>	$op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot op_1$

OP | ~OP

Control Signal Logic - II

<i>aluSignals</i>		
10	<i>isAdd</i> ✓	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1} + \overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}$
11	<i>isSub</i> ✓	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
12	<i>isCmp</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
13	<i>isMul</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
14	<i>isDiv</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
15	<i>isMod</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
16	<i>isLsl</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
17	<i>isLsr</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
18	<i>isAsr</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
19	<i>isOr</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
20	<i>isAnd</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
21	<i>isNot</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$
22	<i>isMov</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1}$